

Topic- Current Electricity

Assignment-6

Subject-Physics

Class-XII

1. Define specific resistance, and give its SI unit. 2
2. Which are conjugate arms in the Wheatstone's bridge? Why? 2
3. State the advantages and disadvantages of potentiometer over voltmeter. 2
4. State and explain principle of potentiometer. 2
5. Describe how a potentiometer is used to compare the e.m.f.'s of two cells by connecting them separately. 2
6. Explain the use of potentiometer for determining the internal resistance of cell. 2
7. State any two sources of errors in meter- bridge experiment. Explain how they can be minimized. 2
8. State Kirchhoff's First Law in electric circuit. State the sign convention. Explain it. 2
9. Explain the use of Wheatstone's meter bridge to determine an unknown resistance. 2
10. In a potentiometer experiment, e.m.f. of a cell is balanced by a length of 150 cm on the potentiometer wire. When the cell is shunted by a 10Ω resistance, the balancing length reduces to 90 cm. What is the internal resistance of the cell? 2
11. A potentiometer wire has a length of 2 m and resistance 10Ω . It is connected in series with resistance 990Ω and a cell of e.m.f. 2V. Calculate the potential gradient along the wire. 3
12. In meter bridge experiment with resistance R_1 , in left gap, x in right gap, null point is obtained at 40 cm left end. With a resistance R_2 in left gap and same resistance x in right gap, null point is obtained 50 cm from left end. Where will be null point if R_1 & R_2 are put first in the left gap and right gap still containing x ? 3
13. The current flowing through external resistance of 2Ω is 0.5A when it is connected to a terminal of a cell. The current reduces to 0.25A when external resistance is 5Ω . Use Kirchhoff's law to find e.m.f. of cell. 3
14. Two cells of e.m.f 1.5 volt and internal resistance 1Ω and the other of e.m.f. 2 volt and internal resistance of 2Ω are connected in parallel to send a current through an external resistance 5Ω . Find the current in each branch. 3
15. A potentiometer wire has a length of 10 m and a resistance 20Ω . Its terminals are connected to a battery of e.m.f. 4V and internal resistance 5Ω . What are the distances at which null points are obtained when two cells of e.m.f. 1.5V and 1.3V are connected so as to (a) assist, (b) oppose each other? 3
16. An unknown resistance x is connected in the left gap and a known resistance R in the right gap of the meter-bridge. The balance point is obtained at 60 cm from the left end of the wire. When R is increased by 2Ω , the balance point shifts by 10 cm. Find x and R. 3

For detail study, numerical problems & conceptual questions click below

<https://www.learnbse.in/important-questions-for-class-12-physics-chapter-3/>